

(An ISO 3297: 2007 Certified Organization)

Vol. 5, Issue 8, August 2016

# Efficient Method of Power Saving Topologically-Compressed with 21Transistor's Flip-Flop Using Multi Mode Switches

Dr.K.Srinivasulu, Mrs.K.Manasa

Professor & HOD, Department of Electronics & Communication Engineering, Narsimha Reddy Engineering College

Maismma guda, Hyderabad, T.S, India

Asst. Professor, Dept. of Electronics and Communication Engineering, Narsimha Reddy Engineering College

Maismma guda, Hyderabad, T.S, India

**ABSTRACT** — The increasing market trends of extremely low power operated handy applications like laptop, electronic gadgets etc requires microelectronic devices with low power consumption. It is obvious that the transistor dimensions continues to shrink and as require for more complex chips increases, power management of such deep submicron based chip is one of the major challenges in VLSI industry. The manufacturers are always targeting for low power designs for the reason that to provide adequate physical resources to withstand against design hurdles and this lead to increases the cost and restrict the functionality of the device. This power reduction ratio is the highest among FFs that have been reported so far. The reduction is achieved by applying topological compression technique, merger of logically equivalent transistors to an eccentric latch structure. Fewer transistors, only three, connected to clock signal which reduces the power drastically, and the smaller total transistor count assures to retain the chip area as conventional FFs. In addition, fully static full-swing operation makes the cell lenient of supply voltage and input slew variation. An experimental chip design with 40 nm CMOS technology shows that almost all conventional FFs are expendable with proposed FF while preserving the same system performance and layout area. The performance of this paper is evaluated on the design simulation using HSPICE simulator.

**KEYWORDS:** Low power systems, Flip-Flops, Topological Compression, Supply Voltage, 32 nm CMOS Technology.

### **1. INTRODUCTION**

The mobile market keeps on expanding. In addition to the conventional mobile phone, digital camera, and tablet PC, development of various kinds of wearable information equipment or healthcare associated equipment has newly prospered in recent years. In those kinds of battery-working equipment, reduction of power is a very important issue, and demand for power reduction in LSI is increasing. Based on such background, various kinds of circuit technique have already been proposed. In LSI, generally more than half of the power is dissipated in random logic, of which half of the power is dissipated by flip-flops (FFs). During the ast dozen years, several low-power FFs have been rushed into development. However, in actual chip design, the conventional FF is still used most often as a preferred FF because of its well-balanced power, performance and cell area.

The purpose of this paper is to present a solution to achieve all of the goals: power reduction without any degradation of timing performance and cell area. propose FF realization with a new methodology.



(An ISO 3297: 2007 Certified Organization)

### Vol. 5, Issue 8, August 2016







Fig. 2. Differential sense-amplifier flip-flop (DiffFF).

the detailed power and performance characteristics are shown.

#### **II. BACKGROUND**

Typical low-power FFs with comparison to a conventional FF shown in Fig. 1. Fig. 2 shows a typical circuit of differential sense-amplifier type FF (DiffFF) [1]–[3]. This type of circuit is very effective to amplify small-swing signals, so is generally used in output of memory circuits. In this FF, however, the effect of power reduction goes down in the condition of lower data activity, because these kinds of circuits have pre-charge operation in every clock-low state. Moreover, if we use reduced clock swing, a customized clock generator and an extra bias circuit are necessary. Fig. 3 shows a circuit of conditional-clocking type FF (CCFF) [4]–[6]. This circuit is achieved from a functional point of view. The circuit monitors input data change in every clock cycle and disables the operation of internal clock if input data are not changed. By this operation, power is reduced when input data are not changed. But unfortunately, its cell area becomes almost double that of the conventional circuit shown in Fig. 1. This article has been accepted for inclusion in a future issue of this journal. Content is final as presented, with the exception of pagination.



Fig. 3. Conditional-clocking flip-flop (CCFF).



Fig. 4. Cross-charge control flip-flop (XCFF).



(An ISO 3297: 2007 Certified Organization)

### Vol. 5, Issue 8, August 2016



Fig.5 Adaptive-coupling flip-flop (ACFF).

And mainly due to this size issue, it becomes hard to use if the logic area is relatively large in the chip. Fig. 4 shows the circuit of cross-charge control FF (XCFF) [7]. The feature of this circuit is to drive output transistors separately in order to reduce charged and discharged gate capacitance. However, in actual operation, some of the internal nodes are pre-set with clock signal in the case of data is high, and this operation dissipates extra power to charge and discharge internal nodes. As a result, the effect of power reduction will decrease. Circuits including pre-set operation have the same problem [8]. The adaptive-coupling type FF (ACFF) [9], shown in Fig.

5, is based on a 6-transistor memory cell. In this circuit, instead of the commonly used double-channel transmissiongate, a single channel transmission-gate with additional dynamic circuit has been used for the data line in order to reduce clock-related transistor count. However, in this circuit, delay is easily affected by input clock slew variation because different types of single channel transmission-gates are used in the same data line and connected to the same clock signal. Moreover, characteristics of single-channel transmission-gate circuits and dynamic circuits are strongly affected by process variation. Thus, their optimization is relatively difficult, and performance degradation across various process corners is a concern. Let us summarize the analysis on previously reported low power FFs. For DiffFF [1] and XCFF [7], pre-charge operation is a concern especially in lower data activity. As regards CCFF [4], its cell area becomes a bottleneck to use. And for ACFF.



Fig. 6. Example of combinational type FF

[9], tolerance for input clock slew variation becomes subject to resolve.

#### **III. DESIGN APPROACH**

In order to reduce the power of the FF while keeping competitive performance and similar cell area, we tried to reduce the transistor count, especially those operating with clock signals, without introducing any dynamic or pre-charge circuit. The power of the FF is mostly dissipated in the operation of clock-related transistors, and reduction of transistor count is effective to avoid cell area increase and to reduce load capacitance in internal nodes. In the conventional FF shown in Fig. 1, there are 12 clock-related transistors. To reduce clock-related transistor counts directly from this circuit is quite difficult. One reason is because transmission-gates need a 2-phase clock signal, thus the clock driver cannot be eliminated. Another reason is that transmission-gates should be constructed by both PMOS and NMOS to avoid degradation of data transfer characteristics caused by single channel MOS usage. Therefore, instead of transmission-gate type circuit, we start with a combinational type circuit as shown in Fig. 6. To reduce the transistor-count based on logical equivalence, we consider a method consisting of the following two steps. As the first step, we plan to have a circuit with two or more logically equivalent AND or OR logic parts which have the same input signal combination, especially including clock signal as the input signals. Then, merge those parts in transistor level as the second step.



(An ISO 3297: 2007 Certified Organization)

#### Vol. 5, Issue 8, August 2016

#### IV. PROPOSED TOPOLOGICALLY-COMPRESSED FLIP-FLOP:

#### 4.1. Proposed FF and Transistor Level Compression

After investigating many kinds of latch circuits, we have set up an unconventionally structured FF, shown in Fig. 7. This FF consists of different types of latches in the master and the slave parts. The slave-latch is a well-known Reset-Set (RS) type, but the master-latch is an asymmetrical single data input type. The feature of this circuit is that it operates in single phase clock, and it has two sets of logically equivalent input AND logic, X1 and Y1, and X2 and Y2. Fig. 8 shows the transistor-level schematic of Fig. 7. Based on this schematic, logically equivalent transistors are merged as follows. For the PMOS side, two transistor pairs in M1 and S1 blocks in Fig. 8 can be shared as shown in Fig. 9. When either N3 or CP is Low, the shared common node becomes VDD voltage level, and N2 and N5 nodes are controlled by PMOS transistors gated N1 and N4 individually. When both N3 and CP are High, both N2 and N5 nodes are pulled down to VSS by NMOS transistors gated N3 and CP. As well as M1 and S1 blocks, two PMOS transistor pairs in M2 This article has been accepted for inclusion in a future issue of this journal. Content is final as presented, with the exception of pagination.







Fig. 8. Transistor level schematic of Fig. 7.



(An ISO 3297: 2007 Certified Organization)

### Vol. 5, Issue 8, August 2016



Fig. 9. Transistor merging in PMOS side.



Fig. 10. Transistor merging in NMOS side.

And S2 blocks are shared. For the NMOS side, transistors of logically equivalent operation can be shared as well. Two transistors in M1 and M2 blocks in Fig. 10 can be shared. Transistors in S1 and S2 are shared as well.



(An ISO 3297: 2007 Certified Organization)

### Vol. 5, Issue 8, August 2016



Fig. 11. Further transistor merging in PMOS side.



Fig. 12. The state of internal nodes.

Further in the PMOS side, CP-input transistors in S1 and S2, shown in Fig. 11, can be merged, because N2 and N3 are logically inverted to each other. When CP is Low, both nodes are in VDD voltage level, and either N2 or N3 is ON. When CP is High, each node is in independent voltage level as shown in Fig. 12. In consideration of this behavior, the CP input transistors are shared and connected as shown in Fig. 11. The CP-input transistor is working as a switch to connect S1 and S2. This process leads to the circuit shown in Fig. 13. This circuit consists of seven fewer transistors than the original circuit shown in Fig. 8. The number of clock-related transistors is only three. Note that there is no dynamic circuit or pre-charge circuit, thus, no extra power dissipation emerges. We call this reduction method Topological Compression (TC) method. The FF, TC Method applied, is called Topologically-Compressed Flip-flop (TCFF).

### 4.2 Cell Operation:

Fig. 14 shows simulation waveforms of the circuit shown in Fig. 13. In Fig. 13, when CP is low, the PMOS transistor connected to CP turns on and the master latch becomes the data input mode. Both VD1 and VD2 are pulled up to power-supply level, and the input data from D is stored in the master latch. When CP is high, the PMOS transistor connected to CP turns this article has been accepted for inclusion in a future issue of this journal. Content is final as presented, with the exception of pagination.



(An ISO 3297: 2007 Certified Organization)

Vol. 5, Issue 8, August 2016



Fig. 13. Transistor level schematic of topologically compressed flip-flop (TCFF).



Fig. 14. TCFF with scan type.



Fig. 15. TCFF with reset type.

off, the NMOS transistor connected to CP turns on, and the slave latch becomes the data output mode. In this condition, the data in the master latch is transferred to the slave latch, and then outputted to Q. In this operation, all nodes are fully static

and full-swing. The current from the power supply does not flow into the master and the slave latch simultaneously because the master latch and the slave latch become active alternately. Therefore, timing degradation is small on cell performance even though many transistors are shared with no increase in transistor size.

#### 4.3 Cell Variation:

LSI designs require FFs having additional functions like scan, reset, and set. The performance and cell area for these cells are also important. TCFF easily realizes these cells with less transistor-count than conventional FFs. The circuit diagrams of TCFF with scan, reset, and set are shown in Figs. 15–17. Each circuit can be designed with similar structure, and these FFs also have three transistors connected to CP so the power dissipation is nearly the same as that of TCFF.

#### 4.4 Multi threshold vdd:

Multiple Vt MOS devices are used to reduce power while maintaining speed. High speed circuit paths are designed using low-V t devices, while the high-Vt devices are applied to gates in other paths in order to reduce sub threshold leakage current. Unlike the multiple-Vdd transformation, In addition, multi-Vt optimization does not change the



(An ISO 3297: 2007 Certified Organization)

### Vol. 5, Issue 8, August 2016

placement of the cells. The footprint and area of low-Vt and high-Vt cells are similar. This enables timing-critical paths to be swapped by low-Vt cells easily. However, some additional fabrication steps are needed to support multiple Vt cells, which eventually lengthens the design time, increases fabrication complexity, and may reduce yield. Furthermore, improper optimization of the design may utilize more low-Vt cells and hence could end up with increased power.

### V. RESULTS

#### **Proposed flip-flop:**

The Case Constant	their										
9,70000n 9,80000n 9,90000n 10,00000n	5.0000 5.0000 5.0000 5.0000 5.0000	5.0000 5.0000 5.0000 5.0000	4.9809 4.9842 4.9875 4.9908								
tdly= 8.3047 avgval= 1.63 maxval= 4.99 f minval= -2.47 f	E-13 targ= 20E+00 from= 08E+00 at= rom= 1.0000E 75E-01 at= rom= 1.0000E	2.0058E-09 1.0000E-09 1.0000E-08 -09 to= 2.1358E-09 -09 to=	trig= 2.0 to= 1. 1.0000E-08 1.0000E-08	050E-09 .0000E-08							
p2pval= 5.23	iob concluded	1.0000E-09	to= 1.	.0000E-08							
*proposed flip- ****** job st	- A-2008.03 3 flop * atistics summ	2-BIT (Feb 2 ary	6 2008) wins thom= 25.	nt ****** .000 temp=	25.000						
total	memory used	469 k	hytes								
# nodes = # diodes= # va device =	30 # element: 0 # bjts 0	s= 47 = 0#	jfets =	0#	mosfets =	44					
analysis	time	# points	tot. iter	conv.iter							
op point dc sweep transient readin errchk setun	0.02 0.02 0.46 0.01 0.01	1 11 101	57 139 4564	24	7 rev=	31					
output	0.00										
total total	cpu time elapsed time	0.56 s 1 s	econds econds								
total total	cpu time elapsed time	0.56 s 1 s	econds econds								,
total total	cpu time elapsed time	0.56 s 1 s UI	econds econds	~				_		•	2:22 PM 7/17/2015
	cpu time elapsed time	0.56 s 1 s HSP UI	econds econds	~						•	2.22 PM 7/17/2015
total total	cpu time elapsed time	0.56 s 1 s UI	econds econds	/			-			•	2:22 PM 7/17/2015
total total	cou time elapsed time	0.56 s 1 s HSP UI 1 costa Help	econds econds							•	222 PM 7/17/2015
total total Waves A-2008.03 (no Panaha Window Mo Na A R R R R R R	cpu time elapsed time	0.56 s 1 s HSP UI	econds econds			Feat I for	A			•	222 PM 7/17/2015
total total total Waves A-2008.05 (coo Eseek Window Me el A R M M V total	cpu time elapsed time	0.56 s 1 s HSP UI	econds econds			Factor and a				•	222 PM 7/17/2015
total total total ( () () () () () () () () () () () () (	cpu time elapsed time	0.56 s 1 s UI UI				Fiox > 6				•	222 PM 7/17/2015
total total total	cpu time elapsed time	0.56 s 1 s 1 s 1 s 1 s 1 s 1 s 1 s 1	econds econds			fux fr recovered	A 250 <sup>1</sup>		5	• • • •	222 PM 7/137/2015
total total total Waves & 2008.03 (200 Beeks Window Me & A R R Window Me List	cou time elapsed t	0.56 s 1 s 1 s 1 s 1 s 1 s 1 s 1 s 1	econds econds			Flox 5 Sergened 4n Tene Tene	X	5 A		•	222 PM 7/17/2015
total total Water A 20003 100 Water A 20003 100		0.56 s 1 s HSP UI NOV 201 2 NO 201 9	econds econds		34	FLAX 5	//		2 50		222 PM 7/17/2015
total total Weeka 20000 100 Weeka 200		0.56 s 1 s 1 s 1 s 1 s 1 s 1 s 1 s 1	econds econds	2		Fox 5	() () () () () () () () () () () () () (		- 5		222 PM 7/17/2015
total total Marcel A 2008 21 20 Evaluar 2008 21 20 Evaluar 2008 21 20 Evaluar 20 Eva		0.55 s 1	econds econds	2	3n		4) 56			- - - - - - - - - - - - - - - - - - -	222 PM 7/17/2015
total total Marcel A 20008 0 200 Enel A 2008 0 2008 0 200 Enel A 2008 0 2008 0 200 Enel A 2008 0		0.56 s 1	econds econds	26	3.6	flox = fo Second of Temportal Control of the Control of the Contro	(A) (2 5 cg (2)) 5 cg (2) (2 (2 (2 (2 (2 (2 (2 (2 (2 (2 (2 (2 (2			- - - - - - - - - - - - - - - - - - -	1 2222 PM 7/17/2015
total total () () () () () () () () () ()			econds econds	28	3n	flax = 6 Terrestant Construction Constructio	(A) (25 mg / 2 5 mg /		a 88		222 PM 7/17/2015
total total () () () () () () () () () ()		0.55 5 15 15 15 15 15 15 15 15 15 1	econds econds		30	Succession of the second secon	5 m (110)				222 PM 7/17/7015
total total Water Action of the second of			econds econds	2 2 2	36	An Tene	50 50 (TML) 50 (TML) 50 (TML) 50 (TML)				222 PM 7/71/2015
	cou time elapsed t		econds econds	2000	3a		5 5 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1				222 PM 7717/dts

Transistor level schematic of topologically compressed flip flop (TCFF):

its Edit Cormat View Malo		
the root country that theils		
9.70000n 5.0000 9.80000n 5.0000 9.90000n 5.0000 10.00000n 5.0000	.0000 7.0843 .0000 7.1001 .0000 7.1275 .0000 7.1549	•
td]y9.8588E-12 targ- 2. avgval- 6.8618E+00 from- maxval= 8.3693E+00 at- from- 1.0000E-0 minval- 4.5036E+00 at- from- 1.0000E-0 p2pval= 3.8657E+00 from-	$\begin{array}{llllllllllllllllllllllllllllllllllll$	
****** job concluded ****** HSPICE A-2008.03 32- ****** *tcff * ****** job statistics summar	IT (Feb 26 2008) winnt ****** tnom= 25.000 temp= 25.000	
total memory used	310 kbytes	
<pre># nodes = 15 # elements= # diodes= 0 # bjts = # va device = 0</pre>	26 0 # jfets = 0 # mosfets = 21	
analysis time	points tot. iter conv.iter	
op point 0.01 dc sweep 0.01 transient 0.36 readin 0.01 errchk 0.01 setup 0.01	1 60 11 99 101 5863 280 rev= 67	



(An ISO 3297: 2007 Certified Organization)

# Vol. 5, Issue 8, August 2016

AvanWaves A-2008.03 Design Eanels Window	(20080226) Measure Config	ration	Loois Help				and the			-	-		a x
A 14 8 2 2	12 2 19 19	19I	(P)					N/A					
WaveList		1	- T	T	1	1	1	"huff"	1			1	
DC+Cv(q)							-						
		6											
	* *	1	*										
			0	în	2n	3n	40	So Lime (In) (TIMF)	60	76	ân	9n	10m
Wave List		1	-		24		-	1011	-				
D0 90 v(tp)	<b>1</b>	4											
		2											
		1	0	In	Zn	3n	40	5n	En	7n	ăn	20	10n
Wave List		10					_	19481					
D010v(n)	<b>1</b>												
		1 2											
	2												
			0	1n	2n	3n	40	5o Time (Iii) (TIME)	6n	7n	ðn	9n	10s
3 🔳 🔇	9 🕑	12	HSP	1	1 💽		-	1	1				2:34 PM 7/17/2015

### **TCFF SCANTYPE:**

The Eat Format Wew Help 9,70000 5,0000 5,0000 5,0024 9,00000 5,0000 5,0000 4,9972 10,00000 5,0000 4,9972 10,00000 5,0000 4,9972 10,00000 5,0000 4,9972 10,00000 5,0000 4,9972 10,0000 5,0000 4,9972 10,0000 5,0000 4,9972 10,0000 5,0000 4,9972 10,0000 5,000 10,000 5,000 10,000 10,000 10,000 10,000 10,000 10,000 10,000 10,	
9.7000n 5.0000 5.0000 5.0524 9.6000n 5.0000 5.0000 4.9951 1000-5.5570E-10 tarps 1.427E-09 trips 2.0000E-09 axaval = 4.840:400 from 1.0000E-09 to 1.0000E-08 axaval = 5.1715E+00 from 1.0000E-09 to 1.0000E-08 mirmal = 2.5347E+00 from 1.0000E-09 to 1.0000E-08 ####al = 2.5347E+00 from 1.0000E-09 to 1.0000E-08 #####al = 2.5347E+00 from 1.000E+09 to 1.0000E-08 #####al = 2.5347E+00 from 1.000E+09 to 1.0000E+08 #####al = 2.5347E+00 from 1.000E+09 to 1.0000E+08 #####al = 2.5347E+00 from 1.000E+09 to 1.0000E+08 #####al = 2.5347E+00 from 1.000E+00 to 1.0000E+08 #####al = 2.5347E+00 from 1.000E+00 to 1.000E+08 #####al = 2.5347E+00 from 1.000E+00 to 1.000E+08 #####al = 2.5347E+00 from 1.000E+00 to 1.000E+08 #####al = 2.5347E+00 from 1.000E+00 to 1.000E+	
fdlw-s.6570E-10         tzys.1.4425E-00         trig.2.0808E-09           wynale 4.840/e00         from         1.0000E-09           savale 5.1715H-00         ts         0.000E-09           froms.1.000E-09         to         1.0000E-09           simmal 2.2547E+00         ts         0.000E-08           #immal 2.2547E+00         ts         1.000E-08           ##xxx160         to         1.000E-08           #************************************	
***** poo statistics summary trom= 23.000 temp= 23.000 total memory used 621 kbytes # nodec= 42 # elements= 65 diddek= 0 # bits = 0 # infets = 0# motfets = 60	
totalmemoryused 611kbytes ≢nodos 42 ≢elements 65 eliddes 0 ≠ bits = 0 ≠ iferts = 0 ≠ moxfets = 60	
# nodes = 42 # elements = 0 # ifets = 0 # mosfets = 60	
# diodes= 0 $#$ bits = 0 $#$ ifets = 0 $#$ mosfets = 60	
# va device = 0	
analysis time # points tot. iter conv.iter	
op point 0.05 1 282 dc.sweep 0.06 11 451 transient 7.93 101 45393 1403 rev= 372	
readrin 0.01 errchk 0.01 setup 0.01 output 0.00	
total cpu time 8.12 seconds total elapsed time 8 seconds	
(	1
🙈 🐃 👩 🍓 🙉 HSP 🦪 💽 🔽 🦳	2:40 PM
	//1//2015

1 M 8 8 8 8 3	2 19 12	P* 9	<u>।</u>				< NA	V N/A					
Nave List	_		1		-	-	128	with scan *		-			
	ea (10)				-	_		_					-
	Voteg			$\sum$									
1			0	1s.	2n	3n	4n	En Time (lin) (TIME)	60	7n	- Des	Sn	1Da
Nava List		10					100	whitesh"	Carlos Carlos		1		
	(a) relaço,	4											
		0 -	0	la la	25	36	4n	5n Time (iin) (TIME)	6n	78	8n	3n	101
Vave List		10	1				768	with scen *					_
	<ul> <li>Voteges (ht)</li> </ul>	1											
		•	0	la.	2n	3n	4n	50 Time (kii) (TIME)	6n	78	ôn	3n	105



(An ISO 3297: 2007 Certified Organization)

## Vol. 5, Issue 8, August 2016

### **TCFF with Reset type TCFF RST:**

tcffwithrst.lis - Notepad	_ 0 <b>_ X</b>
File Edit Format View Help	
9.60000n 5.0000 5.0000 4.9999 9.70000n 5.0000 5.0000 5.0000 9.80000n 5.0000 5.0000 5.0000 9.90000n 5.0000 5.0000 5.0000 9.90000n 5.0000 5.0000 5.0000	
<sup>9</sup> tdlys -9.9849E-10 targs 1.065E-09 trigs 2.0050E-09 avgval= 4.015E4-00 frame 1.0000E-09 tos 1.0000E-08 maxval= 5.0356E+00 at 8.000E-09 frome 1.0000E-09 tos 1.0000E-08 mirval= 1.2504E+00 at 2.0000E-08 frome 1.0000E+09 tos 1.0000E-08 frome 1.0000E+00 tos 1.0000E-08	
***** job concluded ****** HSPICE A-2000.03 32-BIT (Feb 26 2008) winnt ****** *tcff with reset * *tcff vith reset * ******	
total memory used 615 kbytes	
# nodes = 39 # elements= 60 # diodes= 0 # bits = 0 # jfets = 0 # mosfets = 56 # va device = 0	
analysis time # points tot.iter conv.iter	
op point 0.02 1 106 dc.sweep 0.05 11 356	
(falls)ent 0.63 101 4092 2.22 Tev= 33 readin 0.03 setup 0.02 output 0.00	3
total cpu time 0.79 seconds	*
4	Þ.
🔞 🗒 🧕 👜 🐚 时 🧭 🚺 🗊	236 PM 7/17/2015

1 104 8 20 20 20 20 20 20 20 20 20 20 20 20 20	1 -21	22 2 10 10 100 100 100 100 100 100 100 1
farm List.		
		0 to 20 30 00 Transition Mr. 80 No. 100
rene test		
anna Lind.		

### TCFF set tp:

Tel: Ett: Format View Heip 9,60000n 5,0000 5,0000 4,9977 9,70000n 5,0000 5,0000 4,9983 9,9000n 5,0000 5,0000 4,9980 10,00000n 5,0000 5,0000 4,9990 10,00000n 5,0000 5,0000 4,9990 10,00000n 5,0000 5,0000 4,9990 10,00000n 5,0000 5,0000 4,9990 10,00000n 5,0000 5,0000 4,9990 10,00000 5,0000 5,0000 5,0000 5,0000 5,0000 4,9990 10,00000 5,00000 5,0000 5,0000 5,000000 5,0000 5,0000 5,0000 5,0000 5,00000 5,0	
9.60000n 5.0000 5.0000 4.9977 9.0000n 5.0000 5.0000 4.9983 9.0000n 5.0000 5.0000 4.9983 9.0000n 5.0000 5.0000 4.9980 10.00000n 5.0000 5.0000 4.9990 10.00000n 5.0000 4.9990 10.0000n 5.0000 5.0000 5.0000 4.9990 10.0000n 5.0000 5.0000 5.0000 4.9990 10.0000n 5.0000 5.0000 5.0000 4.9990 10.0000n 5.0000 5.0000 5.0000 5.0000 10.0000n 5.00000 5.00000 5.0000 5.0000 5.00000 5.00000 5.0000 5.00000 5.00000 5.0000 5.00000000	
tdly= -1.94686-09 targ= 5.80596-11 trig= 2.00506-09 argyal= 2.90346+00 from= 1.0006-09 to= 1.0006-08 maxwal= 5.372160 att = 8.0066-09	
Information 1.00000-09 for 1.00000-08 invala - 1.03246-00 at 1.04216-09 from = 1.00006-09 for 1.00006-08 graval = 6.30054.00 from = 1.00006-08	
***** JOD CONCIUDED ****** HSPICE A-2008.03 32-BIT (Feb 26 2008) winnt ******	
esses	
****** job statistics summary tnom= 25.000 temp= 25.000	
total memory used 477 kbytes	
# nodes = 37 # elements= 54 # diodes= 0 # bits = 0 # jfets = 0 # mosfets = 50 # va device = 0	
analysis time # points tot.iter conv.iter	
op point 0.52 1 97 dc sweep 0.05 11 198	
transient 6.65 101 47231 1151 rev= 324 readin 0.40 errchk 0.11	
setup 0.06 output 0.08 total cpu time 7.77 seconds	



(An ISO 3297: 2007 Certified Organization)

### Vol. 5, Issue 8, August 2016



VI. CONCLUSION FUTURE SCOPE

This paper analyzes the existed FF topologies and suggested a compressed FF to overcome unnecessary power dissipations occurred in the FF due to their large switching activity. The proposed work may eliminate the problem of CMOS total power dissipation between logic transitions occurred in FFs. Topologically Compressed FF design improves the area utilization also this paper has realized with Layout design tools and the relevant layouts are analyzed and various physical parameters are studied at 40 nm Technology. Such designs are suggested to exhibits a competitive performance with current work.

#### REFERENCES

[1] H. Kawaguchi and T. Sakurai, "A reduced clock-swing flip-flop (RCSFF) for 63% power reduction," IEEE J. SolidState Circuits, vol. 33, no. 5, pp. 807–811, May 1998.

[2] J.-C. Kim, S.-H. Lee, and H.-J. Park, "A low-power halfswing clocking scheme for flip-flop with complementary gate and source drive," IEICE Trans. Electronics, vol. E82-C, no. 9, pp. 1777–1779, Sep. 1999.

[3] M. Matsui, H. Hara, Y. Uetani, L. Kim, T. Nagamatsu, Y. Watanabe, A. Chiba, K.Matsuda, and T. Sakurai, "A 200 MHz 13 mm 2- D DCT macrocell using sense-amplifying pipeline flip-flop scheme," IEEE J. Solid-State Circuits, vol. 29, no. 12, pp. 1482–1490, Dec. 1994.

[4] M. Hamada, H. Hara, T. Fujita, C.-K. Teh, T. Shimazawa, N. Kawabe, T. Kitahara, Y. Kikuchi, T. Nishikawa, M. Takahashi, and Y. Oowaki, "A conditional clocking flip-flop for low power H.264/MPEG-4 audio/ visual codec LSI," in Proc. IEEE CICC, 2005, pp. 527–530.

[5] Y. Ueda, H. Yamauchi, M.Mukuno, S. Furuichi, M. Fujisawa, F. Qiao, and H. Yang, "6.33 mW MPEG audio decoding on a multimedia processor," in IEEE ISSCC Dig. Tech. Papers, 2006, pp. 1636–1637.

[6] B.-S. Kong, S.-S. Kim, and Y.-H. Jun, "Conditional capture flip-flop for statistical power reduction," IEEE J. Solid-State Circuits, vol. 36, no. 8, pp. 1263–1271, Aug. 2001.